

Bandgap Reference Cookbook

By : Abdelrahman Hassan Muhammed

1. Reference Circuits Introduction

- What is reference circuit?


A circuit used to generate a **Stable** DC voltage or current



- Little dependence on process and supply voltage
- Well-defined dependence on temperature : Not necessary independent

- Types of Temperature dependence

- Most process parameters vary with temperature so, if we achieve a temperature independent reference it will be also a process independent
- Reference circuits not necessary to be temperature independent
- Temperature dependence could be
 - Positive temperature coefficient (+ ve TC): Proportional to absolute temperature
 - Negative temperature coefficient (- ve TC): Complementary to absolute temperature
 - Zero temperature coefficient (zero TC): Temperature independent PTAT + CTAT

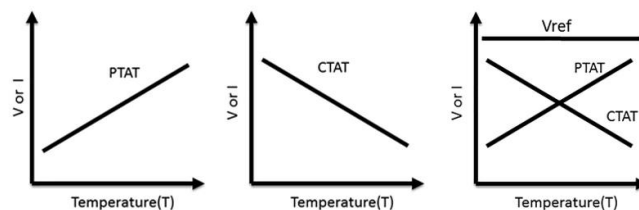


2. Basic operation of BGR (How Vref is ZTAT?)

- Analysis of BGR

→ Using Simple diode model ($V_{BE1} = V_{BE2} = V_{BE}$) and since $V_1 = V_2$ you may expect $I_2 = 0$ but it's invalid approx.

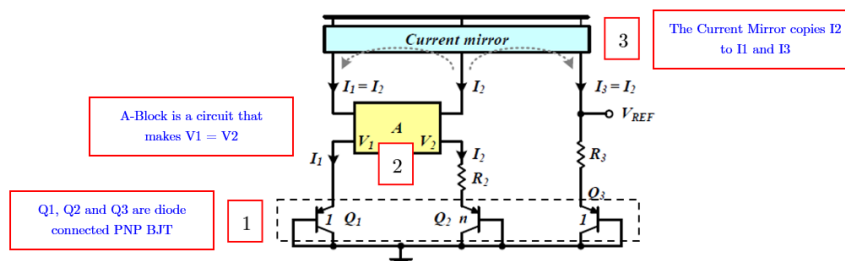→ Q2 is n BJTs diode connected in parallel → $I_{C1} = I_1$ and $I_{C2} = I_2/n$




→ Using BJTs instead of simple diodes because of Accurate spice models and Base connection may provide more design options.

$$I_C = I_S e^{\frac{|V_{BE}|}{V_T}} \rightarrow |V_{BE}| = V_T \ln \frac{I_C}{I_S}$$

$$\Delta V_{BE} = |V_{BE1}| - |V_{BE2}| = V_T \ln n = \frac{KT}{q} \ln n$$

$$I_2 = \frac{\Delta V_{BE}}{R_2} = \frac{KT}{q} \ln n \times \frac{1}{R_2} \rightarrow \therefore I_2 \text{ is a PTAT}$$

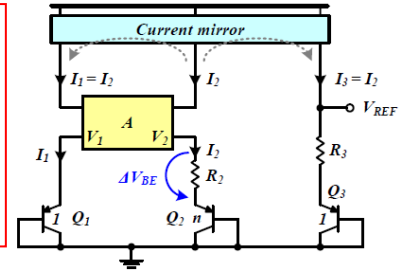
- V_T : the thermal voltage approx. 26mV @ 300k
- I_S : the saturation current and it is constant
- K : Boltzmann's constant
- q : the elementary charge of an electron



$$V_{R3} = I_3 R_3 = \frac{KT}{q} \ln n \times \frac{R_3}{R_2} \rightarrow \text{is a PTAT}$$

$$V_{R3} = 0.086 \ln n \times \frac{R_3}{R_2} \left(\frac{mV}{K} \right) @ 300K$$

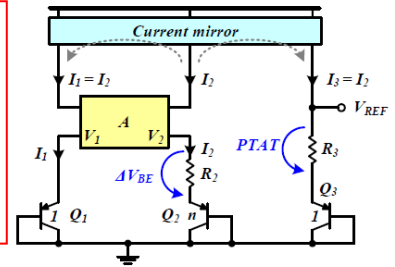Since I3 is a copy of I2 → I3 will be a PTAT current and VR3 will also be a PTAT voltage



It can be shown that $|V_{BE}| = V_T \ln \frac{I_C}{I_S} = V_{G0} - b_1 T$ is a CTAT although I_C and V_T are PTAT but I_S is a strong function of temperature, **Why?**

$$I_S \propto \mu K T n_i^2$$

$$\mu(\text{mobility of holes}) \propto \mu_0 T^m, m \approx -\frac{3}{2} \text{ and } n_i^2 (\text{intrinsic carriers}) \propto T^3 e^{-\frac{E_g(\text{bandgap energy})}{KT}}$$

$$I_S \propto \mu_0 \times T^{m+4} \times K \times e^{-\frac{E_g(\text{bandgap energy})}{KT}}$$

$$I_S = b \times T^{m+4} \times e^{-\frac{E_g(\text{bandgap energy})}{KT}} \rightarrow \text{Strong function of Temperature} \rightarrow |V_{BE}| \text{ is CTAT}$$

Get b1 from simulations: Usually $b1 \approx 1.5 - 2 \text{ mV/K}$

$$V_{ref} = V_{R3} + V_{BE3} = a_1 \times T + V_{G0} - b_1 \times T = V_{G0} \text{ (if } a_1 = b_1)$$

$$V_{G0} = \frac{E_g}{q} \rightarrow \text{Bandgap voltage, it's constant} = 1.2V \text{ at absolute zero kelvin and it is related silicon}$$

- Design Considerations (1)

To design a bandgap we need to determine 3 parameters n , R_2 , R_3


1. **n** : Due to layout considerations, two values of n are usually used $n = 8$ (better matching) and $n = 24$ (better ΔV_{BE})

2. **R_2** : Given current consumption, select R_2 where

$$I_2 = \frac{\Delta V_{BE}}{R_2} = \frac{KT}{q} \ln n \times \frac{1}{R_2}$$

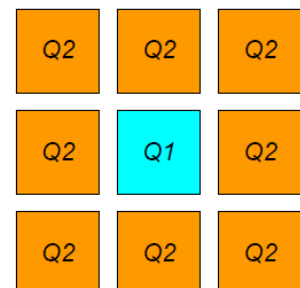
3. **R_3** : Chosen to achieve ZTAT V_{ref} (set $a_1 = b_1$)

$$a_1 = 0.086 \ln n \times \frac{R_3}{R_2} \left(\frac{mV}{K} \right) \text{ and get } b_1 \text{ from simulations}$$



3. Practical CMOS implementation of BGR

- No. 1: Basic Implementation

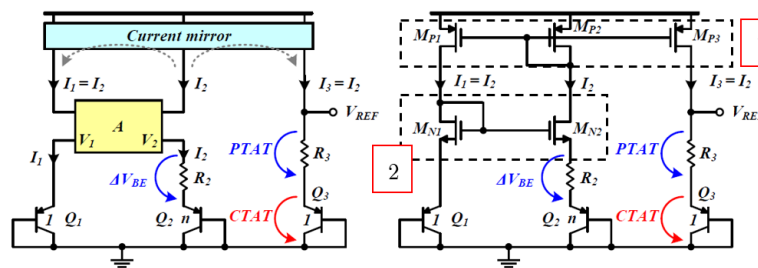

Simple current mirror using M_{P1-3}

A-Block: $M_{N1-2} \rightarrow$ Same Current \rightarrow Same VGS


- Design Consideration (2)

1. Use Large L ($\geq 1\mu m$) is usually used because
2. For low supply voltage, bias the transistors in MI or WI ($g_m/I_D \geq 15$)

- Reduce V_{DS} dependence CLM
- Reduce flicker noise as the low frequency behavior is more important in this circuit
- Large area gives better matching

- No. 2: Op-AMP Implementation

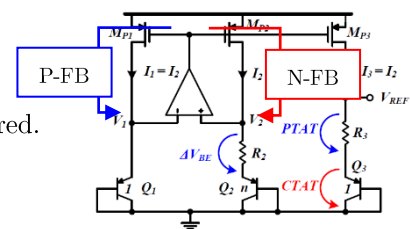- The op amp keeps V_1 and V_2 at the same voltage.
- The op amp can be implemented as a simple 5 T OTA.
- Folded cascode may be used if wide input range is required.
- Bias the op amp using a constant gm circuit. Or use the BGR itself to bias it (self biased)!



Negative or Positive Feedback?

Both Negative and Positive Feedback loop are exist so, we must guarantee $B_N > B_P$


$$B_N = g_{mP2}(R_2 + 1/g_{mQ})$$

$$B_P = g_{mP1}(1/g_{mQ})$$

As R_2 is always +ve Value so, $B_N > B_P$



- This circuit gives $V_{ref} = 1.2 V$ but For modern technologies, this value is higher than V_{DD} itself so, How to get Low Voltage BGR
- The solution is to add PTAT and CTAT in the current domain.

- No. 3: H. Banba's Implementation

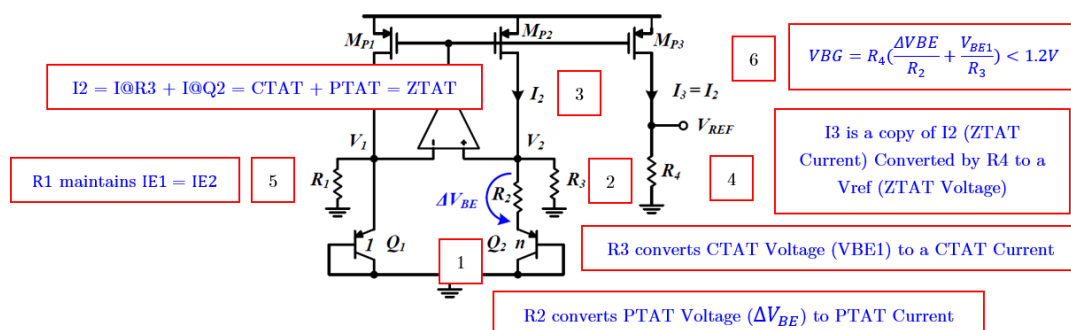

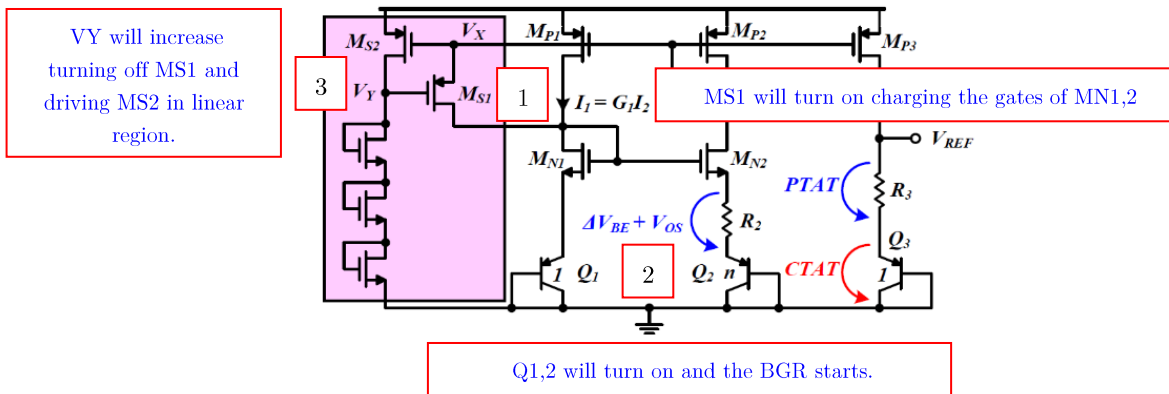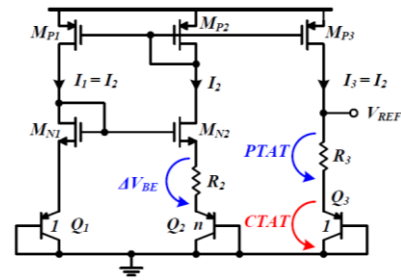4. The Start-up Problem

- All currents = 0 is another valid solution for the circuit!
- Start up circuit must drive the circuit out of the zero bias point, Then it should automatically turn off or consume little current
- Start up verified by ramping up VDD from zero in DC sweep and transient simulations.
- Startup problem means $V_X = V_{DD}$ and $V_Y = 0$



Lets Design